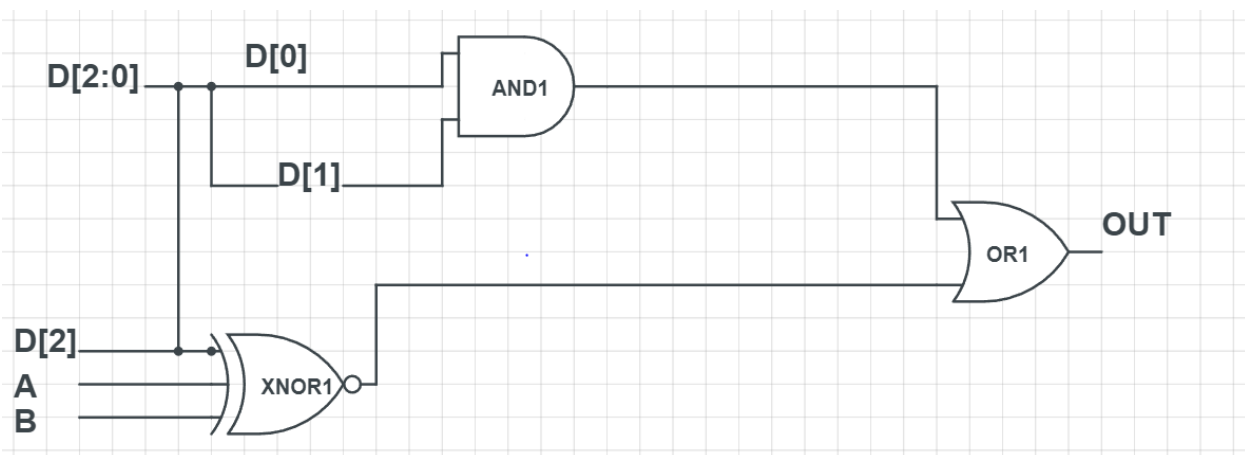


# Assignment 1

Deliverables:


1. Verilog codes for each Design and the top module.
2. Snippets from Model sim simulation wave and results for all possible inputs in the design.

Q1 : Design the following circuit using Verilog




 Q2 :


- 1- Design a half subtractor using gate level modeling style



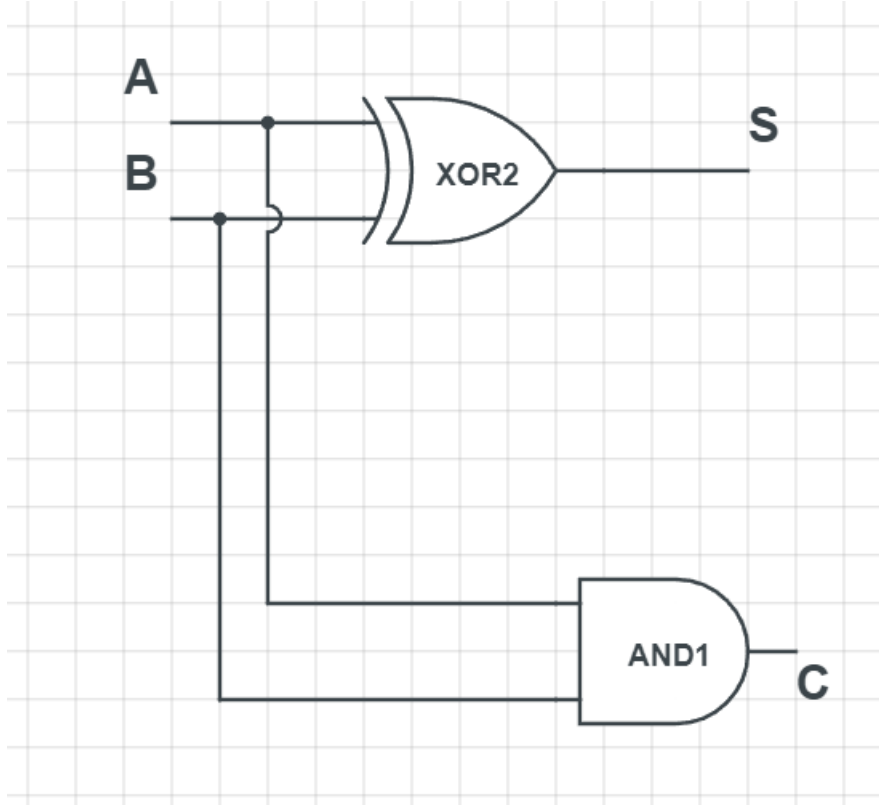2- Design a half adder using gate level modeling



 3- Design this top module and Instantiate the mux written in the session, half adder and half subtractor in your design



**The top module has 3 inputs IN0 , IN1 ,**  
**SEL and 2 outputs SUM , CARRY**