 


Assignment 2

Design the following circuits using Verilog
and create a randomized testbench.


Q1: Design this 3x8 Decoder with enable signal.



Truth Table:

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

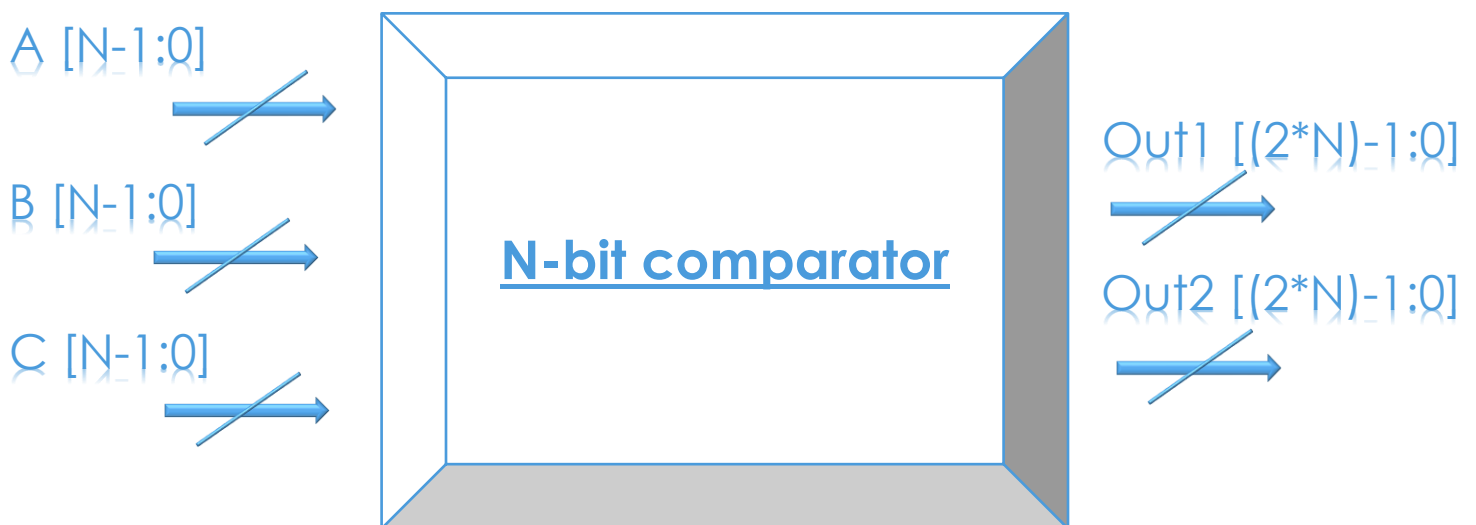Q2: We have 3 inputs N bits (A , B , C) and 2N bits output (out1, out 2) since N is a parameter = 5.





You should compare between three numbers and assign the outputs according to the table below:

Input	Out1	Out2
The largest number And two other inputs	Sign extension of the largest number	Concatenate of the other two inputs
The three inputs are equal	Out1= shift left by 2 of the input	Out2= shift right by 2 of the input
Default	Out1=0	Out2=0

Do we really want to write default case or we covered all possibilities ? Justify your answer.

Sign extension explanation:

Is to check the most significant bit if it was zero then the output will be extended by zeros else will be extended by ones.

